

Name: Keshava Reddy V
ID: COMETFWC054

GATE CS 2010, Majority Function Implementation

Question

For the Boolean function

$$f(P, Q, R) = PQ + QR + PR$$

Find the minterm expansion and implement in hardware.

Question Analysis

- Output is 1 when at least two inputs are 1.
- This is a 3-input Majority Function.
- Canonical expansion required.

The Truth Table

P	Q	R	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Minterms where $F = 1$:

$$m_3, m_5, m_6, m_7$$

Therefore,

$$f(P, Q, R) = m_3 + m_5 + m_6 + m_7$$

Code Uploading Steps

1. Create a PlatformIO project. 2. Write the code in main.cpp inside src folder. 3. Run the project using 'pio run'. 4. Upload using 'pio run -target upload'. 5. Connect Arduino UNO with OTG cable. 6. Observe LED output and verify truth table.

Hardware Implementation

The majority function is implemented using Arduino UNO. Inputs P, Q, R are connected to digital pins. Output F is connected to LED.

Required Components & Pin Connections

Component	Arduino Pin
Input P	Digital 2
Input Q	Digital 3
Input R	Digital 4
Output F (LED)	Digital 8
GND	GND
VCC	5V

Logic Description

- Initialize P, Q, R as digital inputs.
- Compute:
$$F = (P \cdot Q) + (Q \cdot R) + (P \cdot R)$$
- Display result on LED.
- Change inputs as per truth table and verify output.

Experimental Truth Table

P	Q	R	$F(LED)$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Conclusion

- The function outputs 1 when at least two inputs are 1.
- Experimental results match theoretical truth table.
- Hardware implementation confirms majority logic.